

Key words

Capacitance

Free charge

Potential difference

Charging a capacitor

Discharging

In parallel

In series

Equivalent

Energy density

Polar dielectrics




Nonpolar dielectrics

Induced surface charges

Capacitance

$$q = CV$$

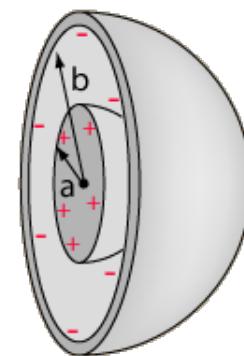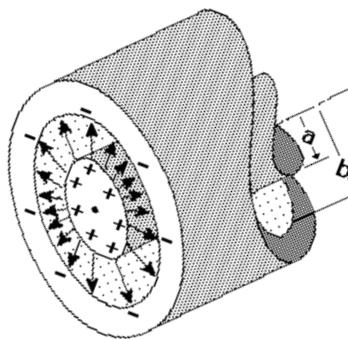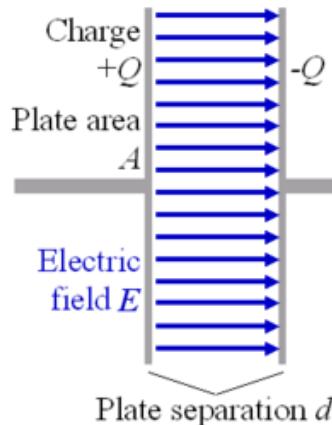q is the free charge
 V is the potential difference between two plates
 C is only dependent on the geometry of the capacitor




$$C = \frac{\epsilon_0 A}{d}$$

$$C = 2\pi\epsilon_0 \frac{L}{\ln(b/a)}$$

$$C = 4\pi\epsilon_0 \frac{ab}{b - a}$$

- 1, Assume charge q on the positive plate
- 2, Calculate the E field between the plates
- 3, Calculate potential difference V between the plates
- 4, $C = q/V$ to find C

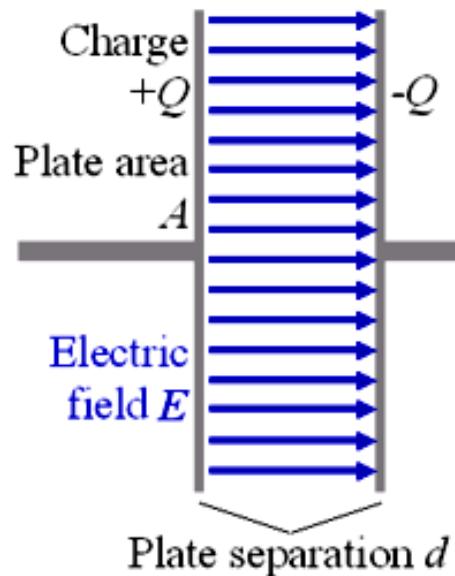Electric field energy / Electric energy density



$$U = \frac{Q^2}{2C} = \frac{1}{2}CV^2 = \frac{1}{2}QV$$

u = Energy density

$$u = \frac{1}{2}\epsilon_0 E^2$$


(electric energy density in a vacuum)

Capacitors in series / parallel connection

Capacitors in series:

- The capacitors have the same charge Q .
- Their potential differences add:

$$V_{ac} + V_{cb} = V_{ab}$$

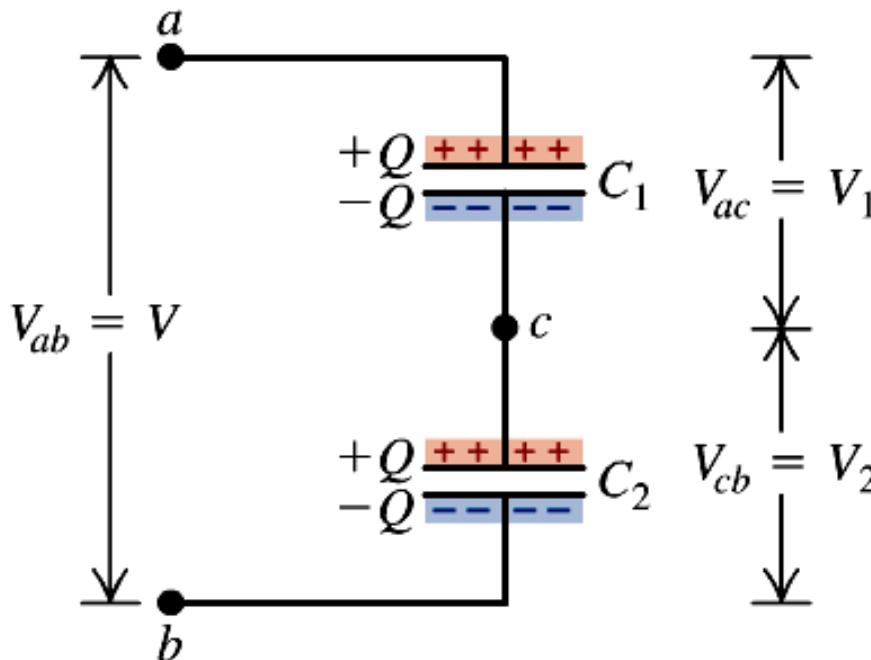

$$V_{ab} = V = V_1 + V_2$$


$$Q_1 = Q_2 = Q$$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \quad (\text{capacitors in series})$$

Capacitors in series / parallel connection

Capacitors in parallel:

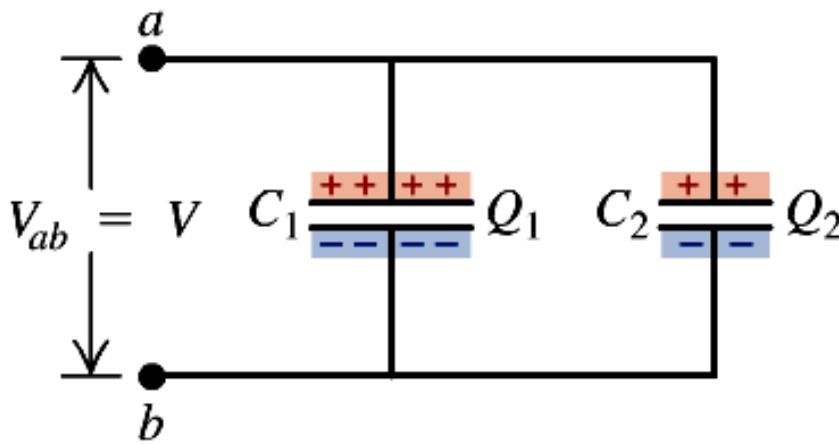- The capacitors have the same potential V .
- The charge on each capacitor depends on its capacitance: $Q_1 = C_1 V$, $Q_2 = C_2 V$.



$$Q = Q_1 + Q_2$$

$$V_1 = V_2 = V$$


$$C_{\text{eq}} = C_1 + C_2 + C_3 + \dots \quad (\text{capacitors in parallel})$$

Question 1

Three uncharged capacitors are connected as shown in the figure. Switch is thrown to the left side until C_1 is fully charged. Then the switch is thrown to the right.

$$Q = CV$$

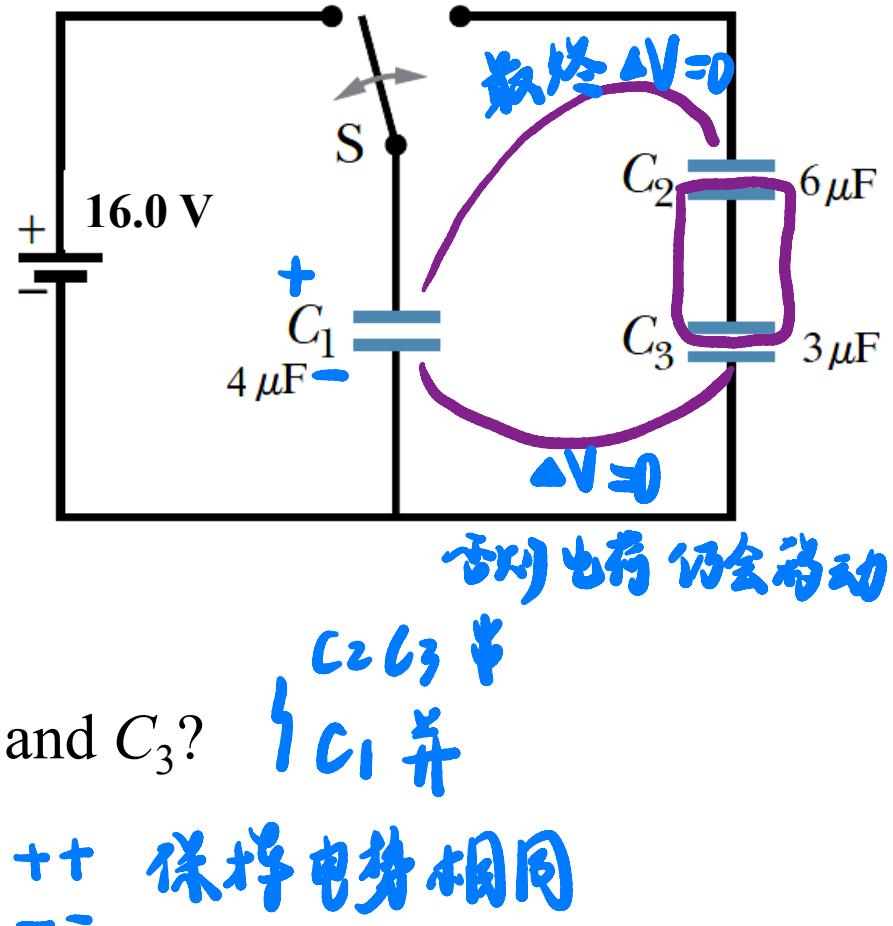What is the final charge on C_1 , C_2 and C_3 ?



Answer:

(a) Solving the two equations

$$\frac{q_1}{C_1} = \frac{q_2}{C_{\text{eq}}} \quad \text{等势}$$

$$q_1 + q_2 = C_1 V_0$$

for q_1 and q_2 , we obtain:
$$q_1 = \frac{C_1^2 V_0}{C_{\text{eq}} + C_1} = \frac{C_1^2 V_0}{\frac{C_2 C_3}{C_2 + C_3} + C_1} = \frac{C_1^2 (C_2 + C_3) V_0}{C_1 C_2 + C_1 C_3 + C_2 C_3}.$$

$$C_{\text{eq}} = 2.00 \mu\text{F} \quad q_1 = 42.7 \mu\text{C}$$



(b) The charge on capacitors 2 is

$$q_2 = C_1 V_0 - q_1 = (4.00 \mu\text{F})(16.0 \text{ V}) - 42.7 \mu\text{C} = 21.3 \mu\text{C}$$

(c) The charge on capacitor 3 is the same as that on capacitor 2:

$$q_3 = C_1 V_0 - q_1 = (4.00 \mu\text{F})(16.0 \text{ V}) - 42.7 \mu\text{C} = 21.3 \mu\text{C}$$

Dielectric and Gauss' Law

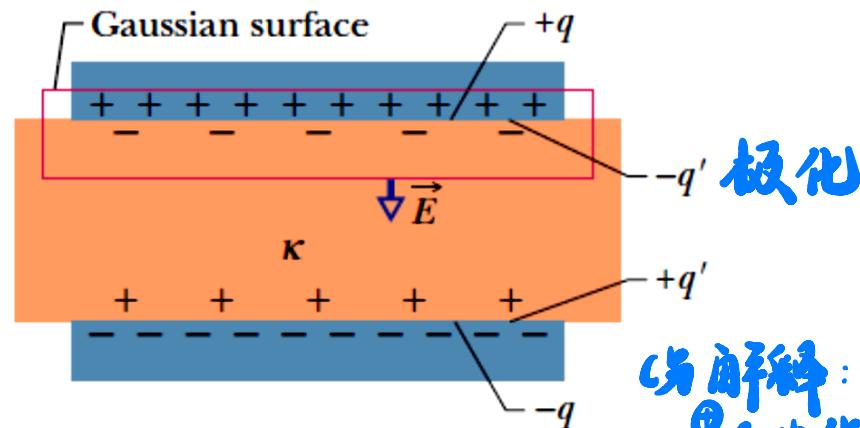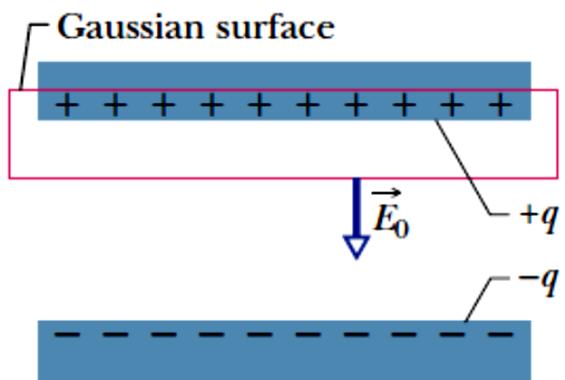

$$C \longrightarrow \kappa C$$

$$\varepsilon_0 \oint \vec{E} \cdot d\vec{A} = \varepsilon_0 E A = q_{enc} = q_f$$

$C = \frac{q}{V}$ → 楊板上自由电荷

$$\left. \begin{aligned} \varepsilon_0 \oint \vec{E} \cdot d\vec{A} &= \varepsilon_0 E A = q_{enc} = q_f - q' \\ \varepsilon_0 \oint \kappa \vec{E} \cdot d\vec{A} &= \varepsilon_0 \kappa E A = q_f \end{aligned} \right\}$$

$$\Rightarrow q_f - q' = \frac{q_f}{\kappa}$$

场解剖：
 ① 电偶极子
 ② 趋向与反向
 ③ Q_E

Question

Capacitance?


$$C = \frac{q}{V}$$
$$\oint \vec{E} \cdot d\vec{A} = \frac{q_f}{k_2 \epsilon_0 A}$$

$$E_2 = \frac{q_f}{k_2 \epsilon_0 A}$$

$$E_1 = \frac{q_f}{k_1 \epsilon_0 A}$$

$$V = E_1 \frac{d}{2} + E_2 \frac{d}{2}$$
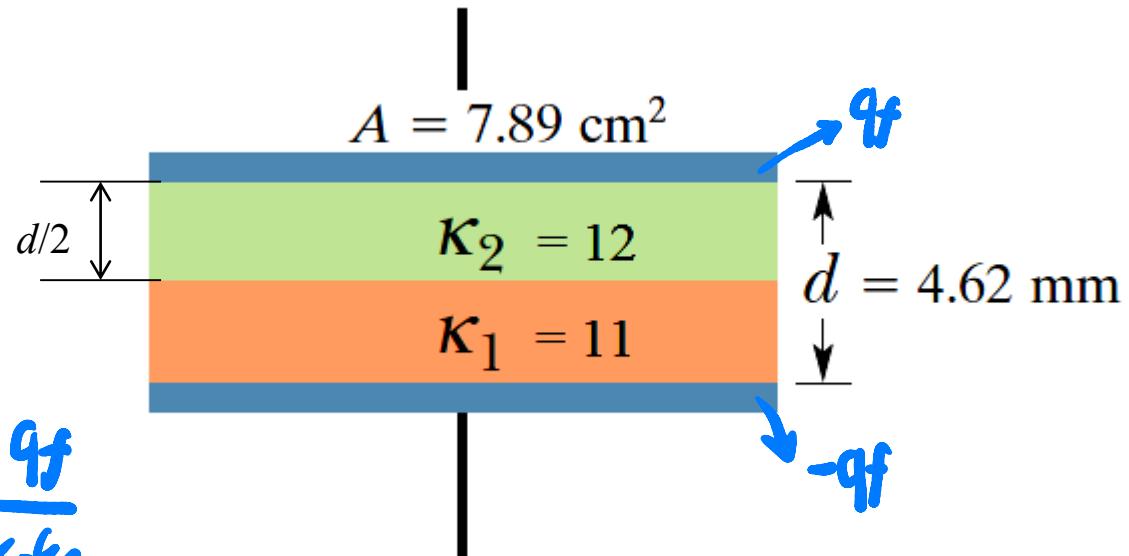
$$C = \frac{q_f}{(\frac{q_f}{k_1 \epsilon_0 A} + \frac{q_f}{k_2 \epsilon_0 A}) \frac{d}{2}} \Rightarrow \frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$



Answer:

We assume there is charge q on one plate and charge $-q$ on the other. The electric field in the lower half of the region between the plates is $E_1 = \frac{q}{\kappa_1 \epsilon_0 A}$,

where A is the plate area. The electric field in the upper half is $E_2 = \frac{q}{\kappa_2 \epsilon_0 A}$.

Let $d/2$ be the thickness of each dielectric. Since the field is uniform in each region, the potential difference between the plates is


$$V = \frac{E_1 d}{2} + \frac{E_2 d}{2} = \frac{qd}{2\epsilon_0 A} \left[\frac{1}{\kappa_1} + \frac{1}{\kappa_2} \right] = \frac{qd}{2\epsilon_0 A} \frac{\kappa_1 + \kappa_2}{\kappa_1 \kappa_2},$$

$$C = \frac{q}{V} = \frac{2\epsilon_0 A}{d} \frac{\kappa_1 \kappa_2}{\kappa_1 + \kappa_2}.$$

This expression is exactly the same as that for C_{eq} of two capacitors in series, one with dielectric constant κ_1 and the other with dielectric constant κ_2 . Each has plate area A and plate separation $d/2$. Also we note that if $\kappa_1 = \kappa_2$, the expression reduces to $C = \kappa_1 \epsilon_0 A/d$, the correct result for a parallel-plate capacitor with plate area A , plate separation d , and dielectric constant κ_1 .


$$C = \frac{2(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(7.89 \times 10^{-4} \text{ m}^2)}{4.62 \times 10^{-3} \text{ m}} \frac{(11.0)(12.0)}{11.0 + 12.0} = 1.73 \times 10^{-11} \text{ F}.$$

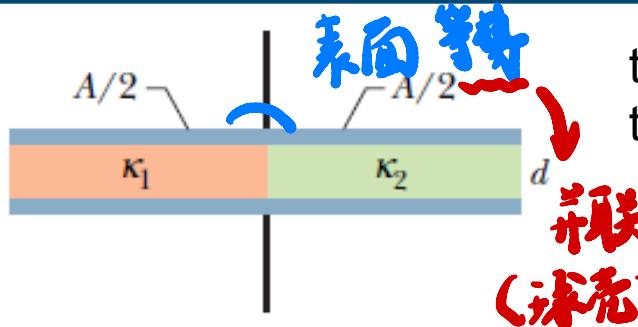Example of Series and parallel for capacitors




the plates of the capacitors are conductor, so
two capacitors in parallel:
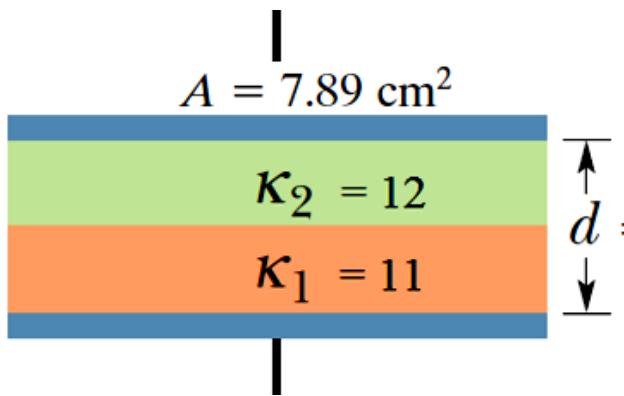
$$C_{eq} = C_1 + C_2 = \kappa_1 \frac{\epsilon_0 A / 2}{d} + \kappa_2 \frac{\epsilon_0 A / 2}{d} = (\kappa_1 + \kappa_2) \frac{\epsilon_0 A}{2d}$$



It can be considered as two capacitors, having same charge q , in series:
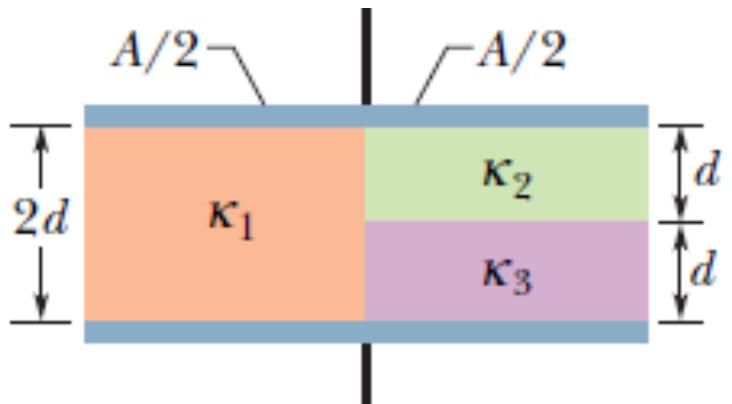
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{d / 2}{\kappa_1 \epsilon_0 A} + \frac{d / 2}{\kappa_2 \epsilon_0 A} \Rightarrow C_{eq} = \frac{\kappa_1 \kappa_2}{(\kappa_1 + \kappa_2)} \frac{\epsilon_0 A}{d / 2}$$




2 and 3 are in series and then parallel with 1, so:

$$C_{eq} = C_1 + C_{23} = \kappa_1 \frac{\epsilon_0 A}{4d} + \frac{\kappa_2 \kappa_3}{(\kappa_2 + \kappa_3)} \frac{\epsilon_0 A / 2}{d}$$

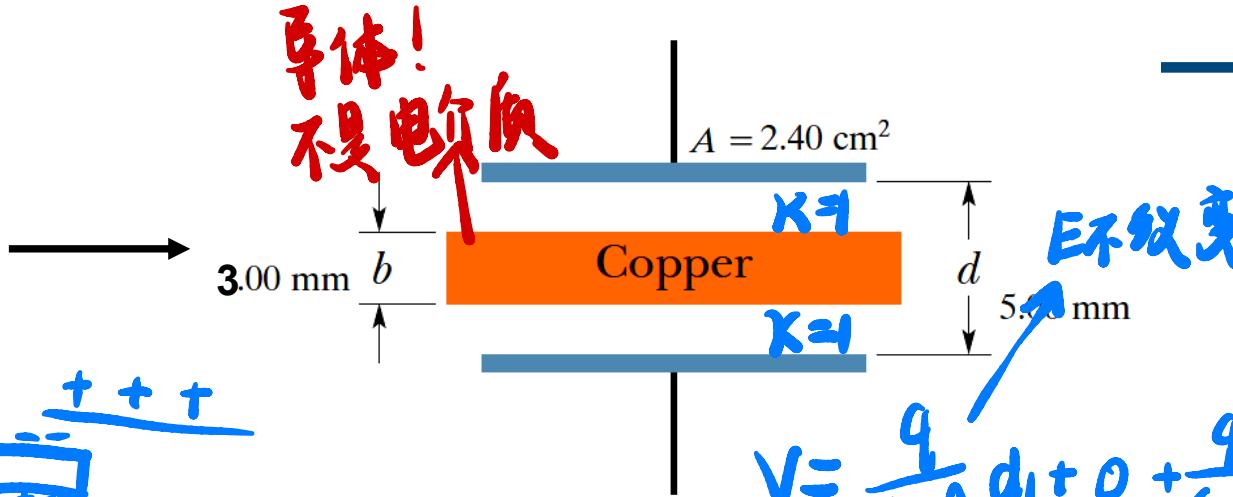Question

Copper is introduced to the isolated parallel capacitor



- (a) Capacitance with the copper introduced?
手写注释: 没有平行板效应啦, 对本题没影响
- (b) If $q = 3.4 \mu\text{C}$ is on the plates, what is the ratio of the stored energy before to that after the copper is inserted? (i.e. $U_{\text{before}} : U_{\text{after}}$)
- (c) How much work is done by applied force on the copper as it is inserted?
- (d) Is the copper sucked in or pushed in?

$$V = \frac{q}{\epsilon_0 A} d_1 + 0 + \frac{q}{\epsilon_0 A} d_2$$
$$C = \frac{q}{V} = \frac{q}{\frac{q}{\epsilon_0 A} (d_1 + d_2)} = \frac{\epsilon_0 A}{d_1 + d_2}$$

Answer:

(a) The length d is effectively shortened by b so $C' = \epsilon_0 A / (d - b) = 1.06 \text{ pF}$.

(b) The energy before, divided by the energy after inserting the slab is


$$\frac{U}{U'} = \frac{q^2 / 2C}{q^2 / 2C'} = \frac{C'}{C} = \frac{\epsilon_0 A / (d - b)}{\epsilon_0 A / d} = \frac{d}{d - b} = \frac{5.00}{5.00 - 3.00} = 2.50.$$

(c) The work done is

$$W = \Delta U = U' - U = \frac{q^2}{2} \left(\frac{1}{C'} - \frac{1}{C} \right) = \frac{q^2}{2\epsilon_0 A} (d - b - d) = -\frac{q^2 b}{2\epsilon_0 A} = -8.16 \text{ J}$$

(d) Since $W < 0$, the slab is sucked in.

Question 3

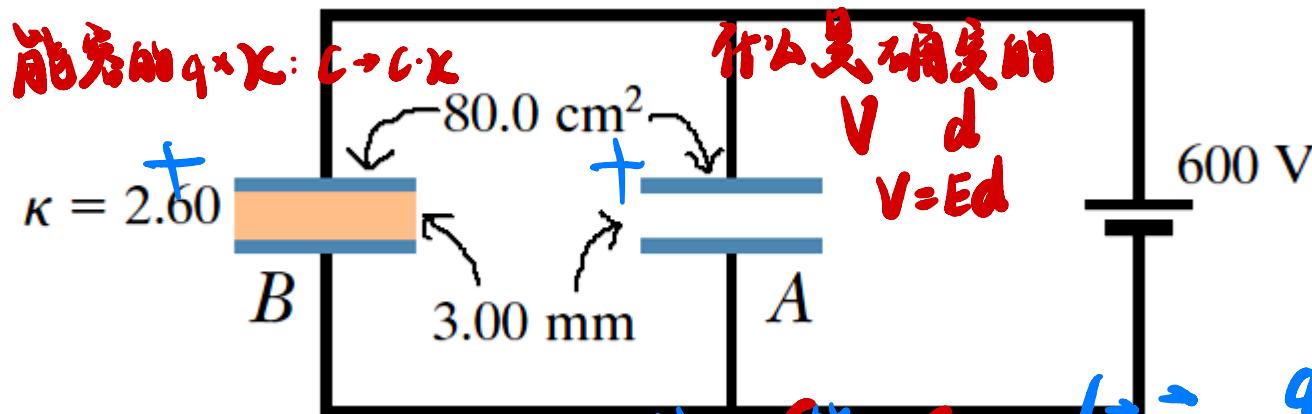

Find

- (a) E-field in the dielectric of capacitor B
- (b) E-field in capacitor A
- (c) Free charge density σ_f on the higher potential plate of capacitor A and capacitor B
- (d) What is the induced charge density σ' on the top surface of the dielectric?

Answer:

- (a) $Ed = V$, since V and d are constant, E is the same.

Since the field is constant and the capacitors are in parallel (each with 600 V across them) with identical distances ($d = 0.00300 \text{ m}$) between the plates, then the field in A is equal to the field in B :

$$|\vec{E}| = \frac{V}{d} = 2.00 \times 10^5 \text{ V/m} .$$

- (b) $|\vec{E}| = 2.00 \times 10^5 \text{ V/m}$. See the note in part (a).

- (c) For the air-filled capacitor,

$$\sigma = \frac{q}{A} = \epsilon_0 |\vec{E}| = 1.77 \times 10^{-6} \text{ C/m}^2 .$$

For the dielectric-filled capacitor,:
 $\downarrow \chi E A = \frac{q_m}{\epsilon_0}$

$$\sigma = \kappa \epsilon_0 |\vec{E}| = 4.60 \times 10^{-6} \text{ C/m}^2 .$$

净荷数相等 induced 是抵消原电场的

Answer:

(d) Capacitor *B* has a relatively large charge but only produces the field that *A* produces (with its smaller charge). We see that the difference in charge densities between parts (c) and (d) is due to the (negative) layer of charge at the top surface of the dielectric; consequently,

$$\sigma' = (1.77 \times 10^{-6}) - (4.60 \times 10^{-6}) = -2.83 \times 10^{-6} \text{ C/m}^2 .$$

Or we can use the following equation:



$$\sigma_{fB} - \sigma' = \frac{\sigma_{fB}}{\kappa} \Rightarrow \sigma' = \left(1 - \frac{1}{\kappa}\right) \sigma_{fB} = 2.83 \times 10^{-6} \text{ C/m}^2$$

So the induced charge density σ' on the top surface of the dielectric is:

$$-\sigma' = -2.83 \times 10^{-6} \text{ C/m}^2$$

A similar example

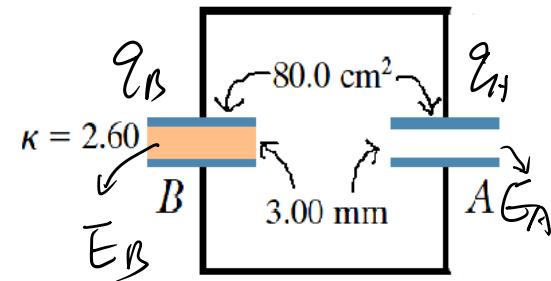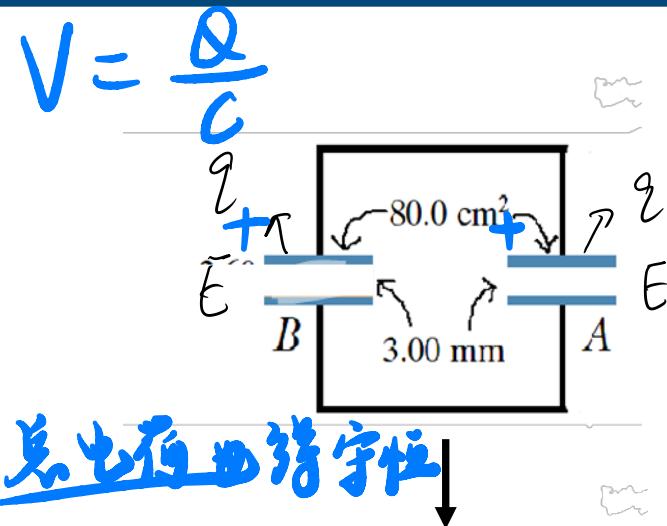Two identical capacitors, each with charge q and E between the plates, are shown in figure. If a dielectric slab is inserted into one of the capacitor. After reaching to a new equilibrium state, what is the free charge on the two capacitors?



Explanation


$$q_{Af} + q_{Bf} = 2q$$

$$q_{Af} = CV$$

$$q_{Bf} = KC \cdot V$$

$$\Rightarrow \begin{cases} q_{Bf} = Kq_{Af} \\ q_{Bf} + q_{Af} = (1+k) \cdot CV = 2q \end{cases}$$


V $\frac{1}{2}$

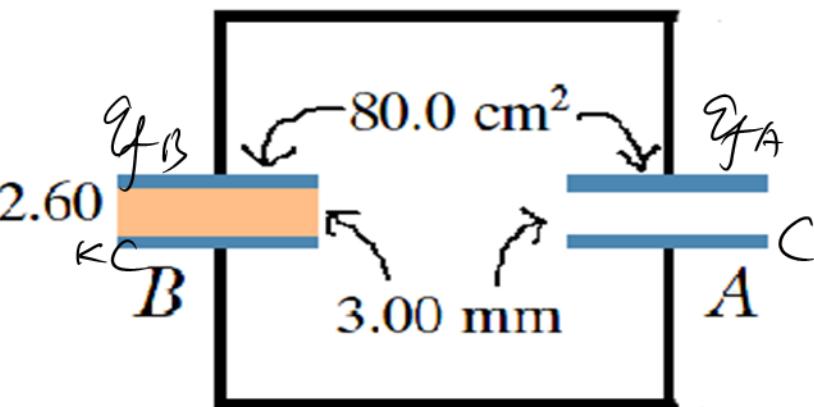

$$\Rightarrow V = \frac{2q}{(1+k)C} \Rightarrow E = \frac{2q}{(1+k) \cdot C \cdot d} = \frac{2q}{(1+k)A_S}$$

$$\therefore q_{Af} + Kq_{Af} = 2q \Rightarrow q_{Af} = \frac{2q}{1+k}, q_{Bf} = \frac{k}{1+k} 2q$$

Try it after class

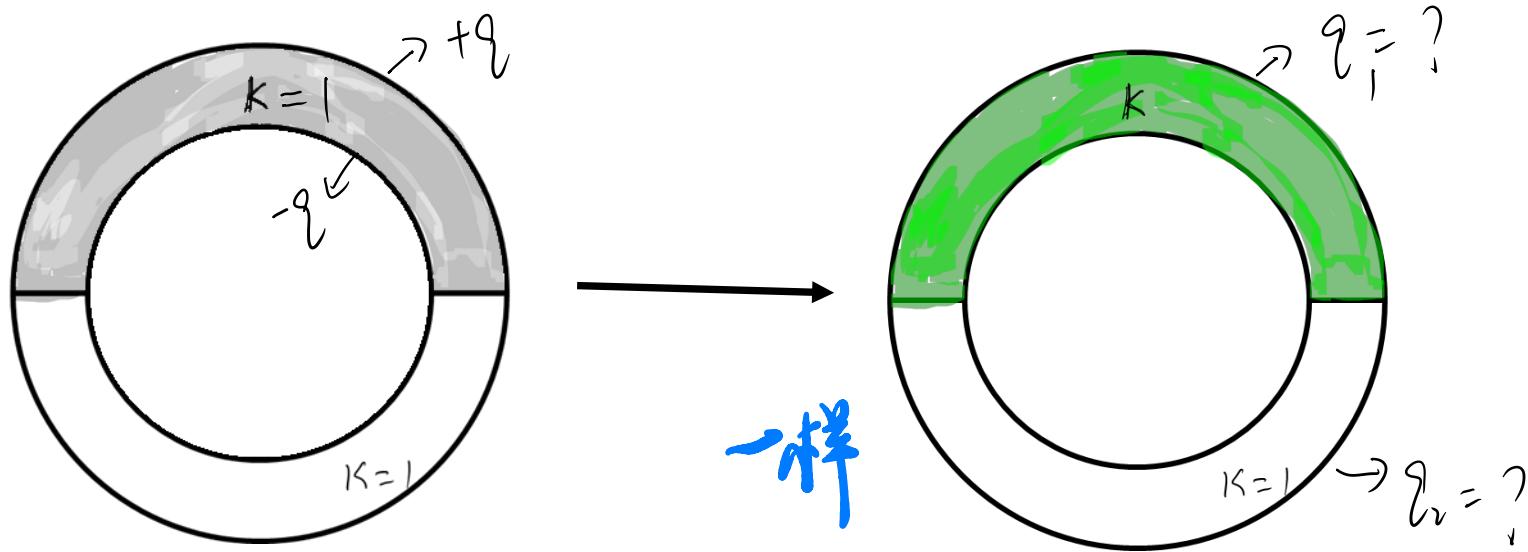

The charge on an isolated spherical capacitor shown in left is q . If a dielectric is filled in the upper half of the capacitor, what are the charge q_1 on the upper half and q_2 on the lower half surface of the capacitor after reaching a new equilibrium state.